

TUTORIAL 3: Logic Gates Overview

1. For a 2-input NOR gate functioning as a negative-AND gate, output X is HIGH if both inputs A and B are HIGH.

FALSE

TRUE / FALSE

2. A two-input XNOR gate will produce a HIGH output when both inputs are equal.

TRUE

$$A=0, B=0$$

$$A=1, B=1$$

$$X=0+1=1$$

$$X=1+0=1$$

TRUE / FALSE

3. A NOR gate with inverters at the inputs has the same logic function as an AND gate.

$$\overline{A+B} = AB$$

TRUE

TRUE / FALSE

4. A 2-input NAND gate and a 2-input NOR gate produces the same output when both inputs are HIGH.

$$X=0$$

$$X=0$$

TRUE

TRUE / FALSE

5. The _____ gate produces a HIGH output when all inputs are LOW.

a) NOR

b) NAND

c. XOR

d. AND

6. A 2-input logic gate **X** produces a HIGH output when input A is LOW and input B is HIGH. Which of the following is **NOT** logic gate X? **OR**

a. OR

0 1 1

b) NOR

0 1 0

c. NAND

0 1 1

d. XOR

0 1 1

7. Complete the following questions:

i) Draw the logic symbol of an XOR gate.




ii) Give appropriate labels to the inputs and output.

iii)



A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

iii) Write its truth table.

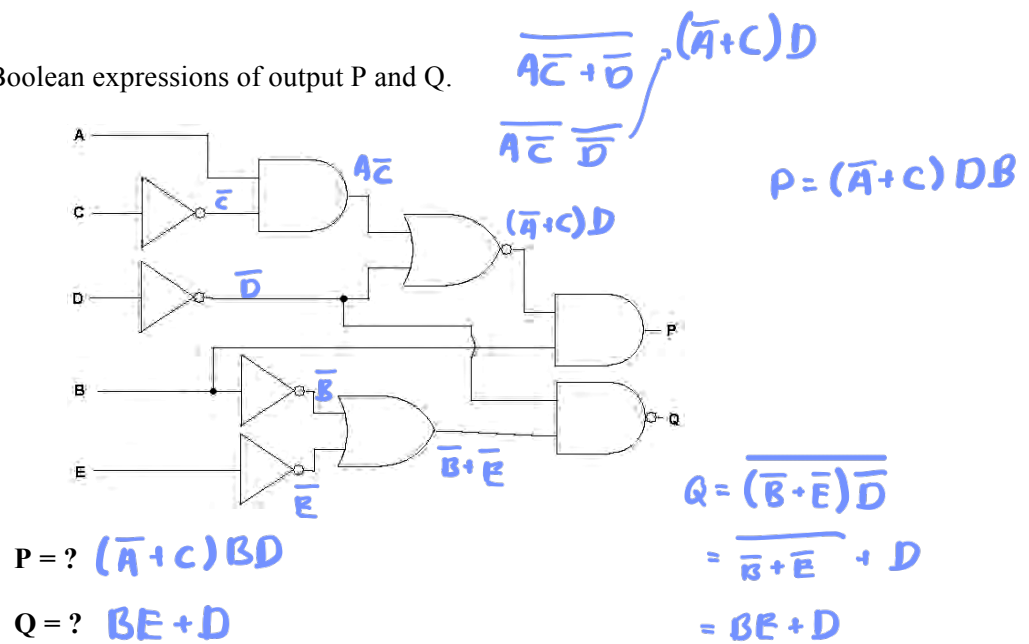8. Write the Boolean expressions of output P and Q.




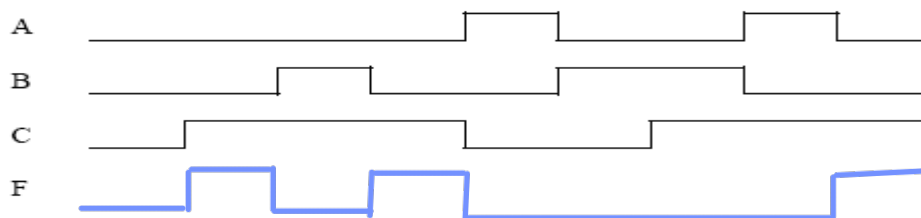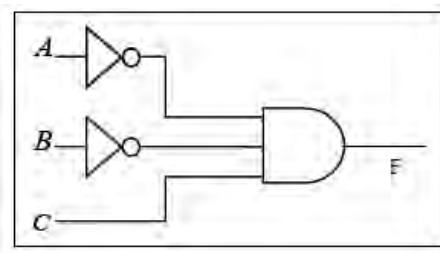9. Complete the timing diagram based on the given input for the following logic diagram.



10. Draw symbol for the following gates:

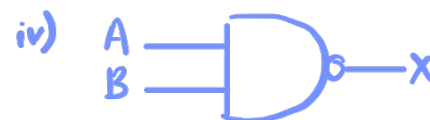- i) ii) 2-input OR gate
- ii) iii) Inverter
- iv) 2-input NAND gate
- v) 2-input NOR gate



11. Given an AND gate with 3 inputs, what should the input values be to get an output of 1 (HIGH)? *All high input (1)*


12. Given an OR gate with 3 inputs, what should the input values be to get an output of 1 (HIGH)? *At least 1 high input (1)*

13. Fill in the table below, follow the example given.

Gate	Input			Output
	A	B	C	
AND	1	0	1	$X = ABC = 0$
OR	0	1	0	$X = A + B + C = 1$
AND	1	1	1	$X = ABC = 1$
OR	0	0	0	$X = A + B + C = 0 + 0 + 0 = 0$
NOR	1	1	1	$X = \bar{A} + \bar{B} + \bar{C} = 0$
AND	1	0	0	$X = ABC = 0$

14. Given the input waveform(s) below, show the appropriate output waveform, X , with a timing diagram.

- i) XNOR
- ii) XOR
- iii) NAND

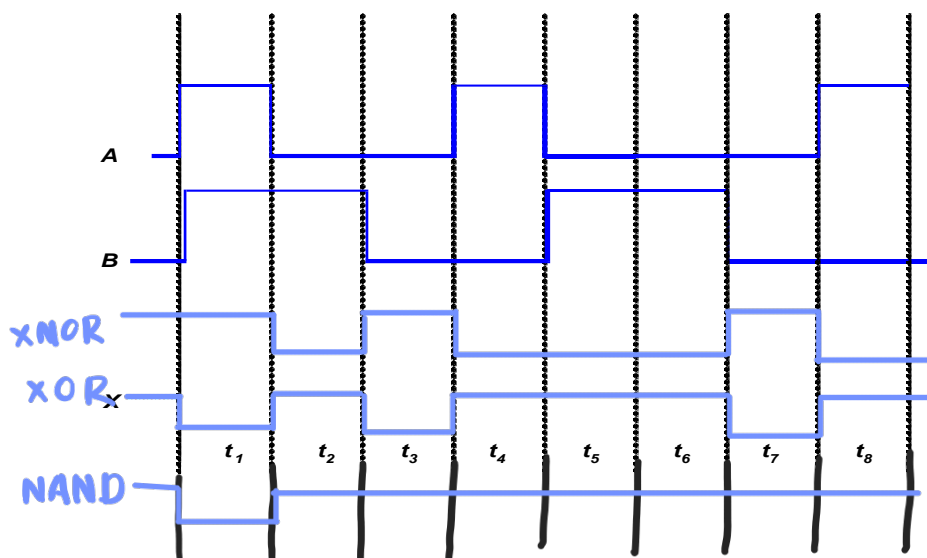

15. Identify the following devices according to logic function:

- i) 74LS04 *Hex inverter*
- ii) 74ALS10 *Triple 3-input NAND gate*
- iii) 74HC00 *Quad 2-input NAND gate*

16. Given the logic gates below, write the logic expression for it.

