

1. What are the **equations** to retrieve the sum (Σ) and the carry output (C_{out}) of a full adder?

$$\Sigma = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + (A + B)C_{in}$$

2. How **many full adders** are needed to complete these additions?


- a. 101 and 010 **3**
- b. 1100 and 0101 **4**
- c. 111 and 001 **3**
- d. 1010 and 1101 **4**
- e. 010 and 011 **3**
- f. 11001 and 10101 **5**

3. For Question 3 (Show your workings):

$$101 + 010$$


- a. Draw the block diagram of parallel adders for Question 3
- b. Get *every instance* of sum (Σ) and carry output (C_{out}) for each full adder.
- c. Get the results.

a)

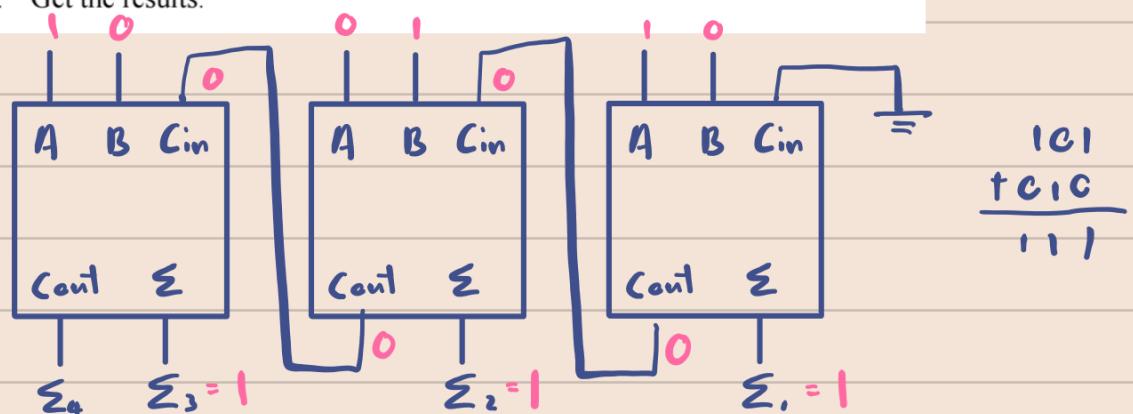


$$\Sigma = 111$$

b)

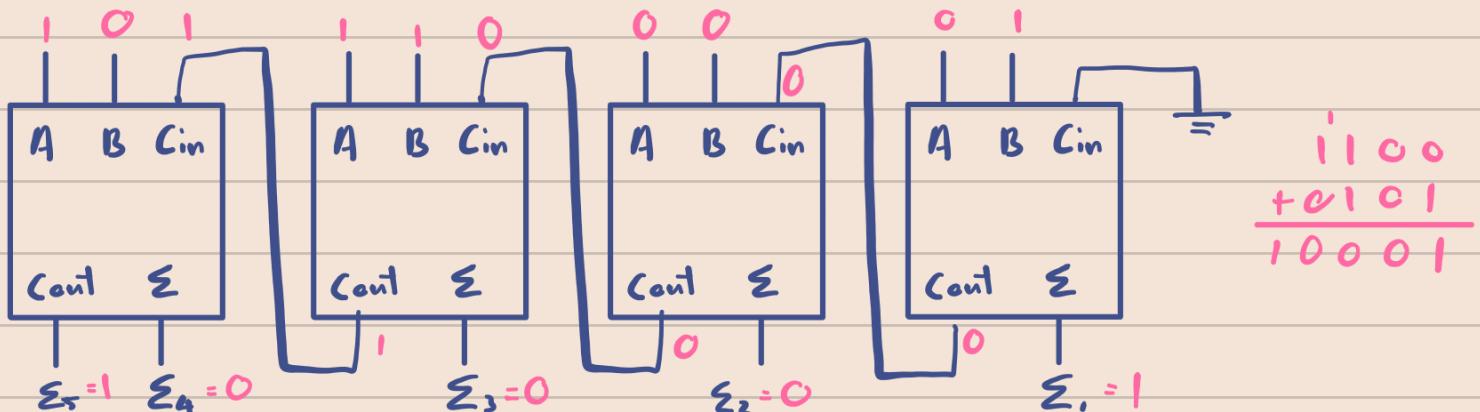

$$\Sigma = 10001$$


c)

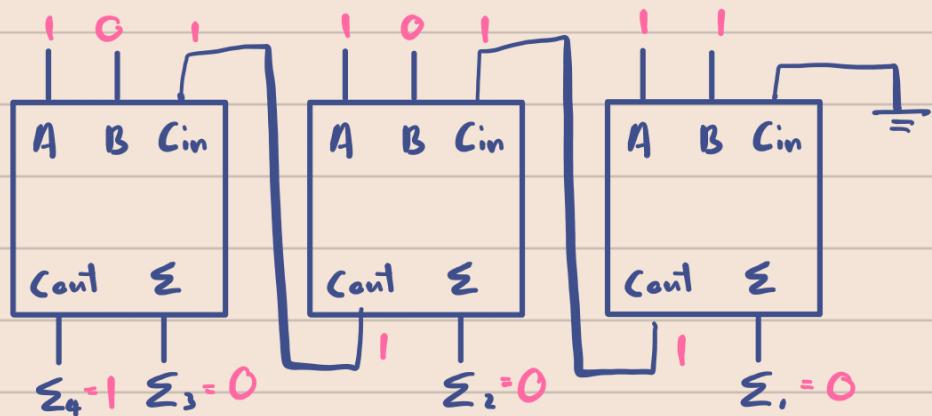

$$\begin{array}{r}
 111 \\
 +001 \\
 \hline
 1000
 \end{array}$$

$$\Sigma = 1000$$


d)

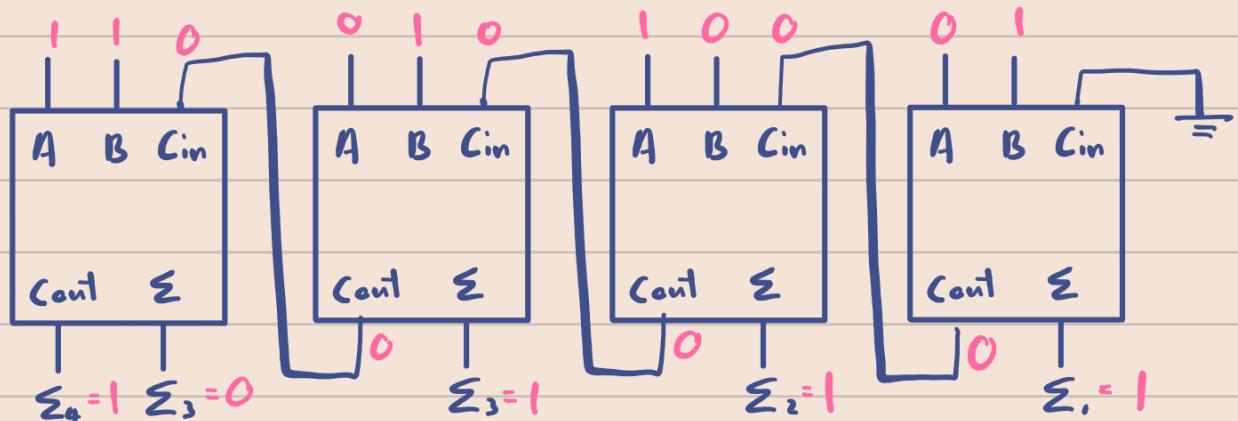

$$\begin{array}{r}
 1010 \\
 +1101 \\
 \hline
 10111
 \end{array}$$

$$\Sigma = 10111$$

e)

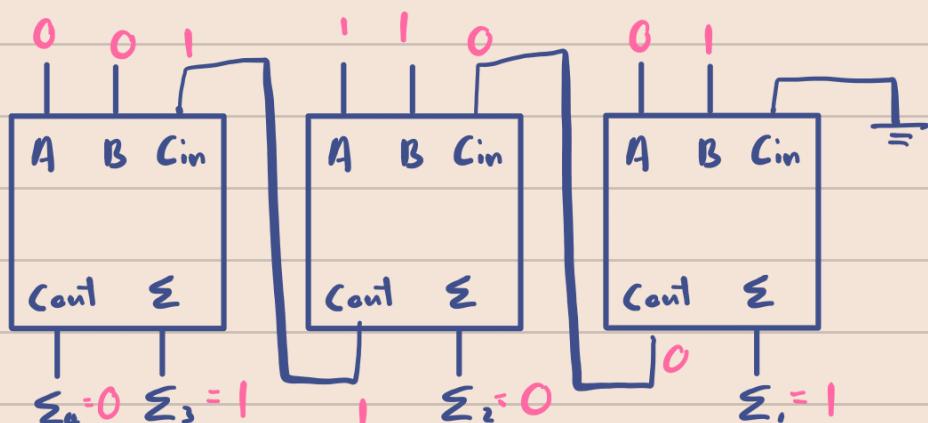


$$\begin{array}{r}
 010 \\
 +011 \\
 \hline
 101
 \end{array}$$

$$\Sigma = 101$$

$$\begin{array}{r}
 11001 \\
 +10101 \\
 \hline
 101110
 \end{array}$$

f)

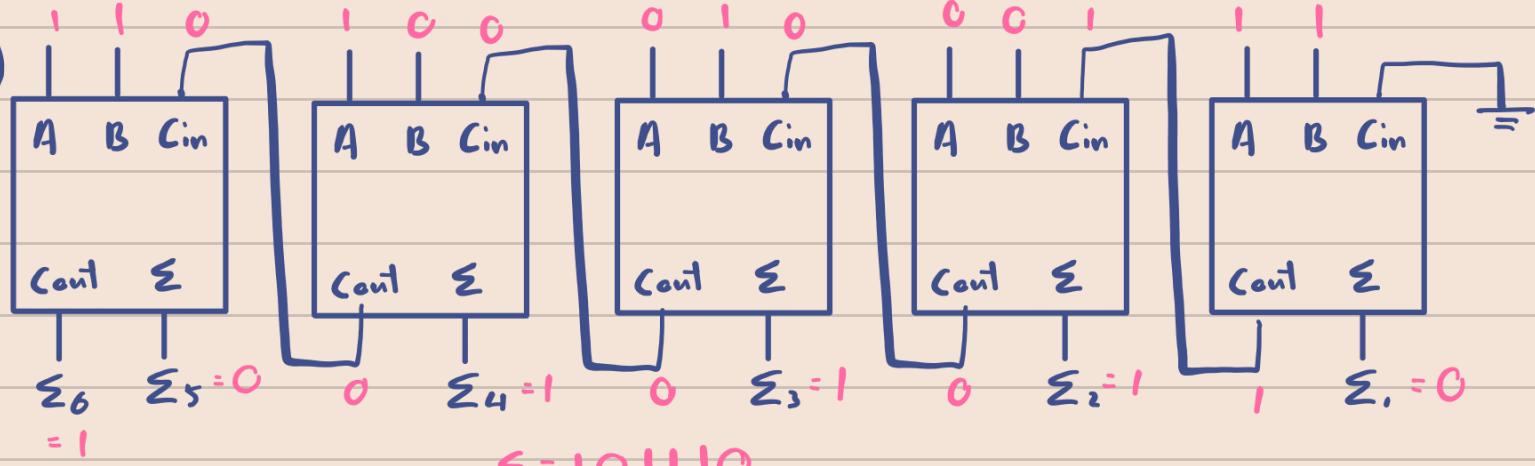

$$\Sigma = 101110$$

4. Use the parallel adder truth table (Table 1) to find the sum and output carry for the addition of the following two 4 bit number if the input carry (C_{n-1}) is 0. Show the diagram.


$$X_4 X_3 X_2 X_1 = 1101$$

$$Y_4 Y_3 Y_2 Y_1 = 0101$$

Table 1


X_n	Y_n	C_{n-1}	C_n	Σ_n
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1
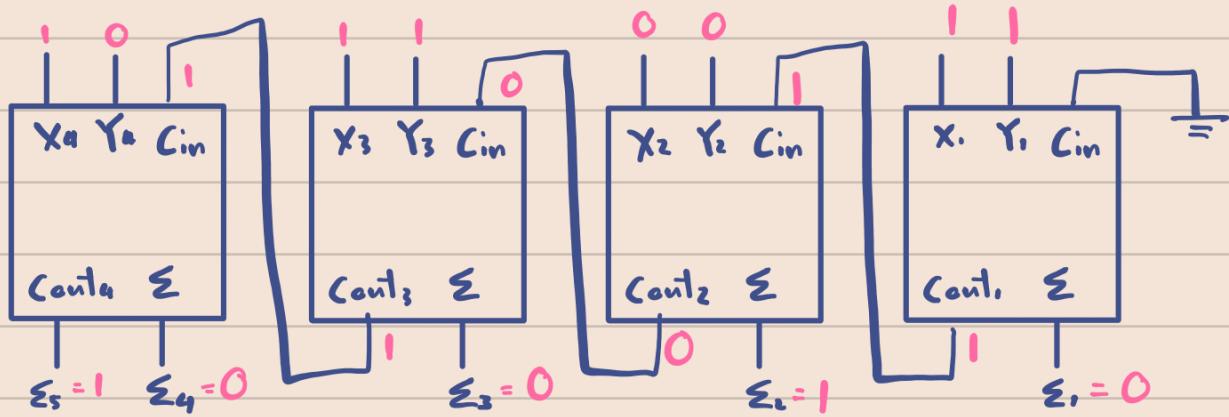
$$\begin{array}{r}
 1 \ 1 \ 0 \ 1 \\
 + 0 \ 1 \ 0 \ 1 \\
 \hline
 1 \ 0 \ 0 \ 1 \ 0
 \end{array}$$



$$\Sigma = 10010$$

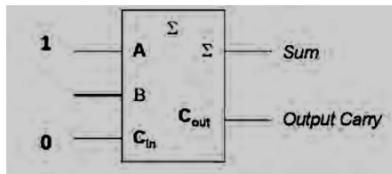5. Determine the outputs of **Sum** and **Output Carry** for the inputs given for Full Adder as shown below.




If $B=0$	If $B=1$
$\Sigma = 1$	$\Sigma = 0$
$Cout = 0$	$Cout = 1$

7. Convert the following:


- 98 in BCD to binary
- 01110101 in BCD to binary

$$\begin{aligned}
 a) 98 &= 1001 \ 1000 = 01100010 \\
 b) 0111 \ 0101 &= 75 = 01001011
 \end{aligned}$$

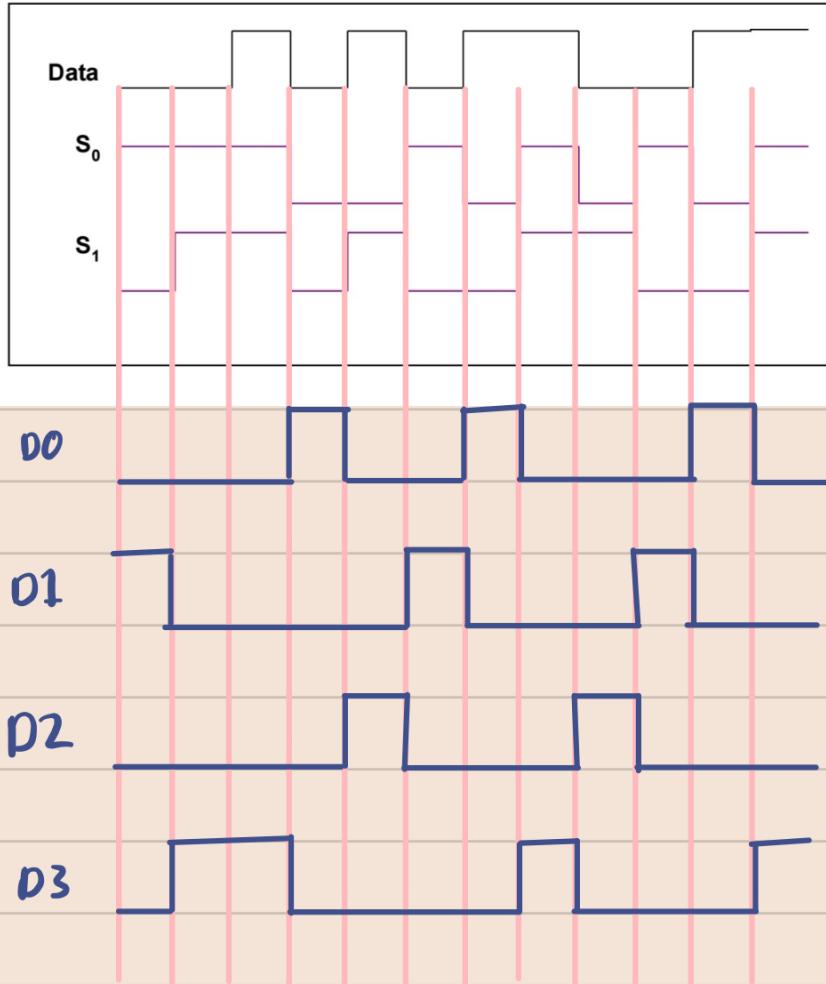8. A DEMUX has 4 outputs D0, D1, D2 and D3. Given the information below, draw the appropriate waveforms for the outputs.



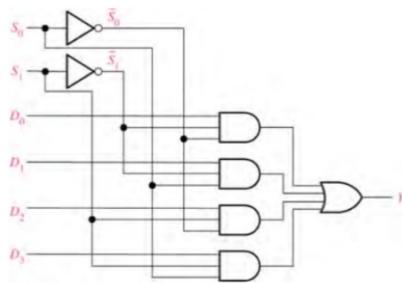9. a) What type of multiplexer shown in a figure below.
 b) Develop the truth table for multiplexer in figure below.



a) 1x4 multiplexer

10. What is the difference between **decoder** and **multiplexer**.

Decoder - detect the presence of a specified combination of bits on its input

Multiplexer - allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination.

12. Using a full-adder, determine the logic state (1 or 0) at each gate output for the following inputs:

- (a) $A = 1, B = 1, C_{in} = 1$
- (b) $A = 0, B = 1, C_{in} = 1$
- (c) $A = 0, B = 1, C_{in} = 0$

a) $\Sigma = 1, C_{out} = 1$

$\Sigma = 0, C_{out} = 1$

$\Sigma = 1, C_{out} = 0$

13. What the full-adder inputs that will produce each of the following outputs:

- (a) $\Sigma = 0, C_{out} = 0$
- (b) $\Sigma = 1, C_{out} = 0$
- (c) $\Sigma = 1, C_{out} = 1$
- (d) $\Sigma = 0, C_{out} = 1$

a) $A = 0, B = 0, C_{in} = 0$

b) $A = 1, B = 0, C_{in} = 0$

c) $A = 1, B = 1, C_{in} = 1$

d) $A = 1, B = 1, C_{in} = 0$

14. Determine the outputs of a full-adder for each of the following inputs:

- (a) $A = 1, B = 0, C_{in} = 0$
- (b) $A = 0, B = 0, C_{in} = 0$
- (c) $A = 0, B = 1, C_{in} = 1$
- (d) $A = 1, B = 1, C_{in} = 1$


a) $\Sigma = 1, C_{out} = 0$

b) $\Sigma = 0, C_{out} = 0$

c) $\Sigma = 0, C_{out} = 1$

d) $\Sigma = 1, C_{out} = 1$


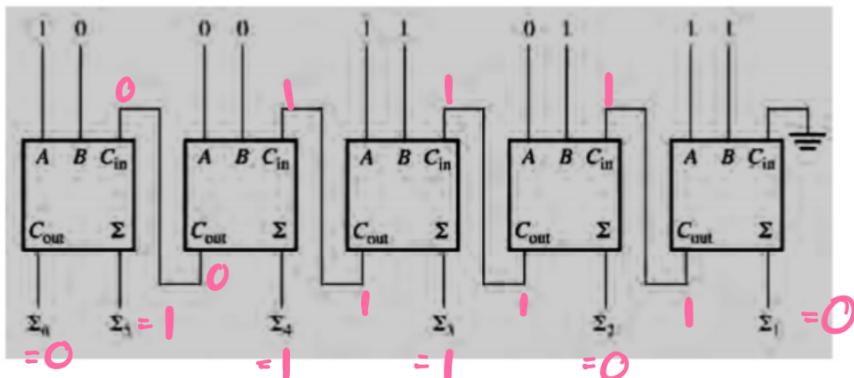
15. For the parallel-adder, determine the complete sum by analysis of the logical operation of the circuit. Verify your result by longhand addition of the two input numbers.



$$\begin{array}{r}
 10101 \\
 + 00111 \\
 \hline
 11100
 \end{array}$$

$\Sigma = 11100$

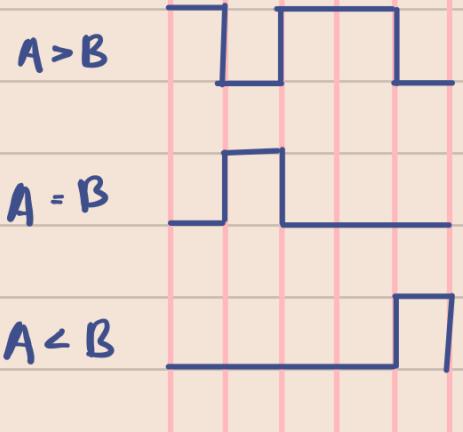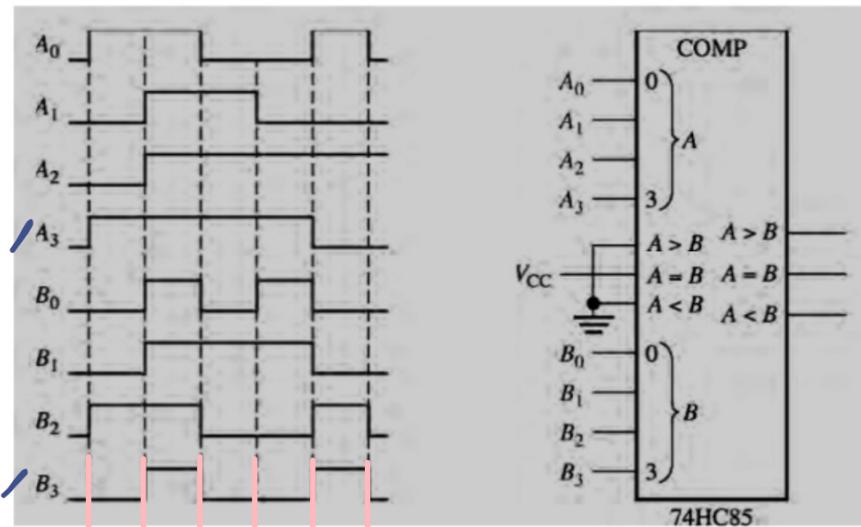16. For the 4-bit comparator, plot each output waveform for the inputs shown. The outputs are active-HIGH.



17. Show the decoding logic for each of the following codes if an active-HIGH (1) output is required:

- (a) 1101 $A\bar{B}CD$
- (b) 1000 $A\bar{B}\bar{C}\bar{D}$
- (c) 11011 $A\bar{B}\bar{C}DE$
- (d) 11100 $A\bar{B}C\bar{D}\bar{E}$
- (e) 101010 $A\bar{B}C\bar{D}EF$
- (f) 111110 $A\bar{B}CDEF$
- (g) 000101 $\bar{A}\bar{B}CDEF$
- (h) 1110110 $A\bar{B}CDEF\bar{G}$

10c1

cc11

18. For the decimal-to-BCD encoder logic, assume that the 9 input and the 3 input are both HIGH. What is the output code? Is it a valid BCD code?


10c1 cc11, valid because they are between 0-9.

19. Convert the following decimal numbers to BCD and then to binary.

- (a) $2 = 0010 = 0010_2$
- (b) $8 = 1000 = 1000_2$
- (c) $13 = 00010011 = 1101_2$
- (d) $26 = 00100110 = 11010_2$
- (e) $33 = 00110011 = 100011_2$

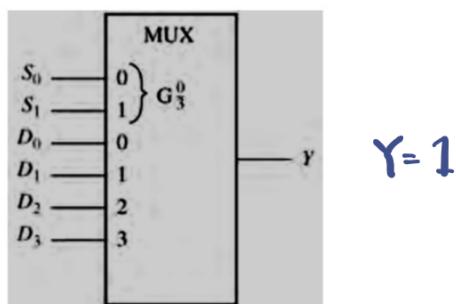20. For the multiplexer given, determine the output for the following input states:


$$D_0 = 0, D_1 = 1, D_2 = 1, D_3 = 0, S_0 = 1, S_1 = 0.$$



$$Y = 1$$


21. Draw a logic circuit for 2-to-1 multiplexer (MUX) using gates.

S_0	Y
0	D_0
1	D_1

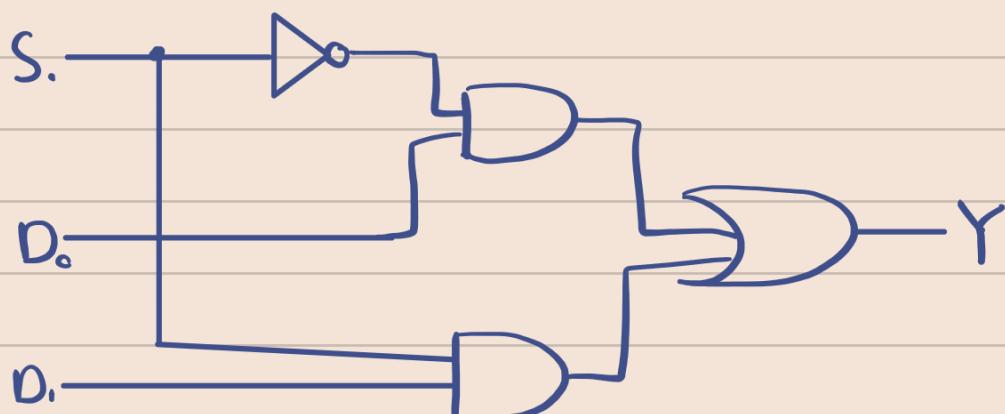


22. (a) Show how two 2-to-1 MUX (with no added gates) could be connected to form a 3-to-1 MUX. Input selection should be as follows:
 If $AB = 00$, select I_0
 If $AB = 01$, select I_1
 If $AB = 10$ - (B is a don't care), select I_2


A	B	I_0	I_1	I_2
0	0	1	x	x
0	1	x	1	x
1	0	x	x	1
1	1	x	x	1

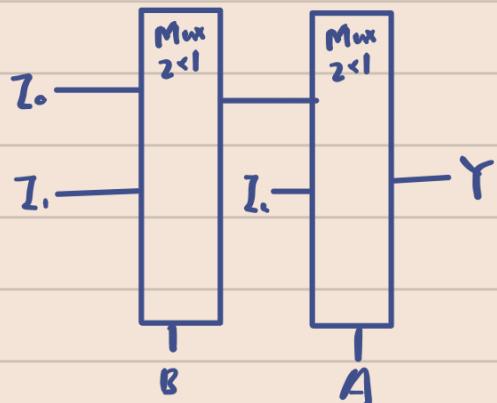

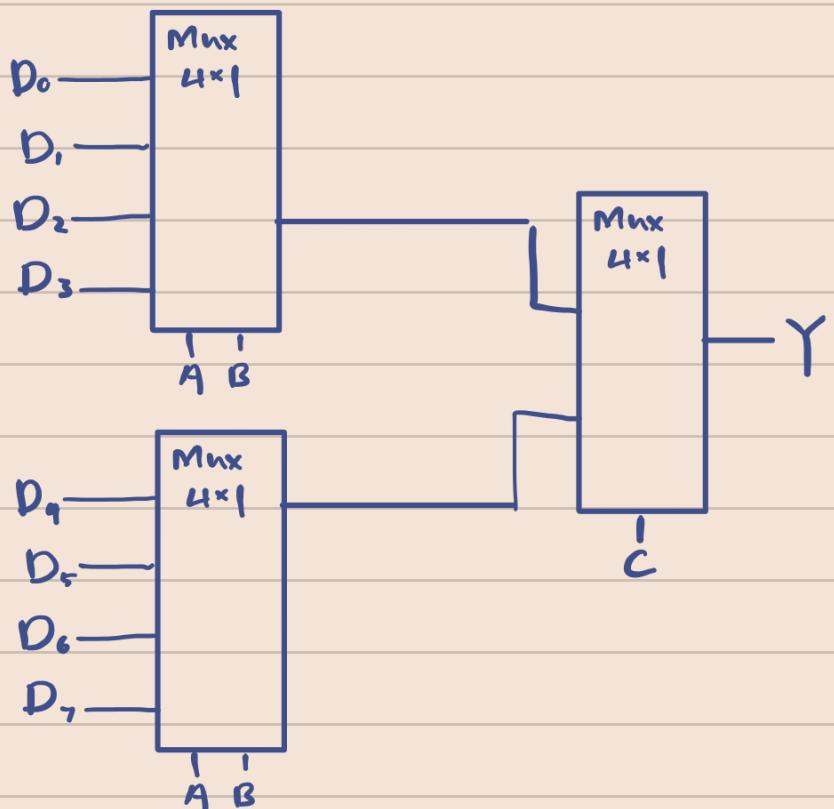- (b) Show how two 4-to-1 and one 2-to-1 MUX could be connected to form an 8-to-1 MUX with three control inputs.



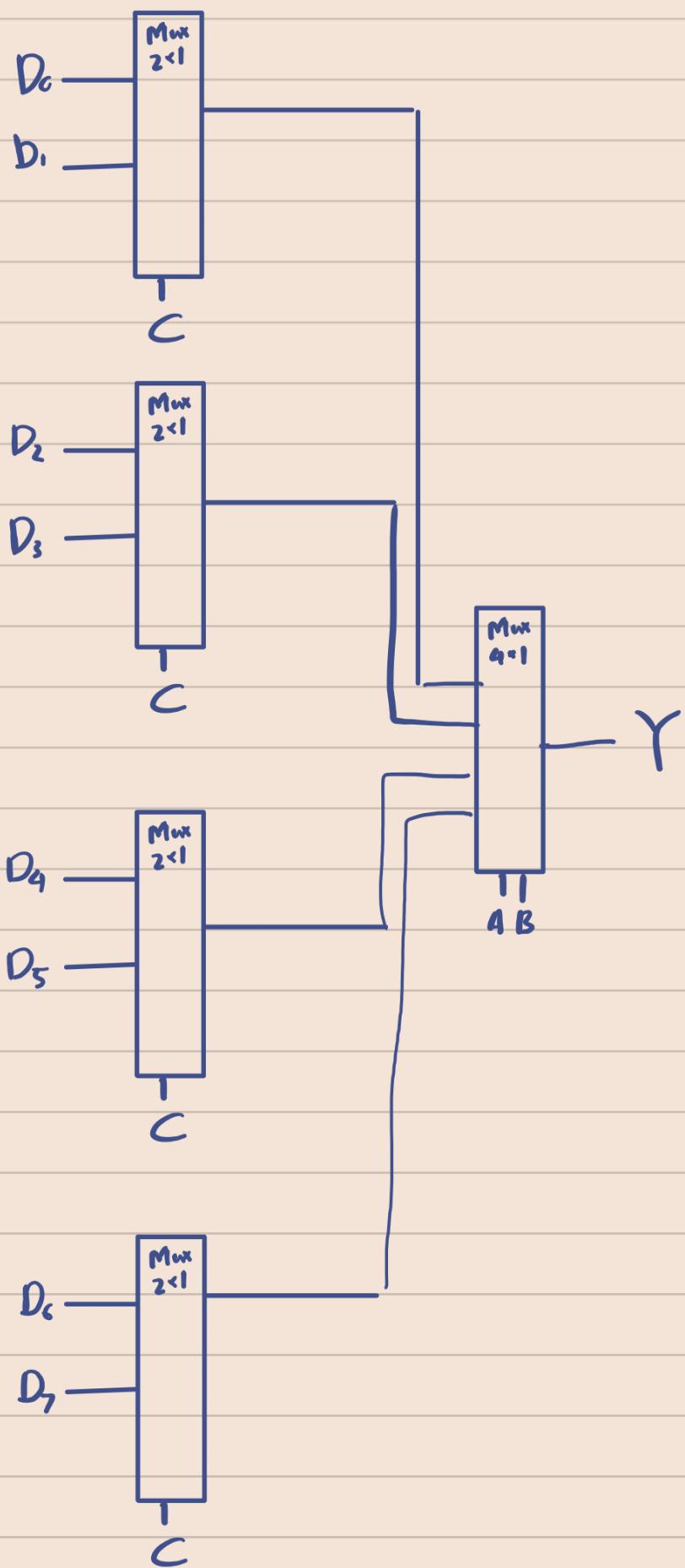
- (c) Show how four 2-to-1 and one 4-to-1 MUX could be connected to form an 8-to-1 MUX with three control inputs.



24. Realize a full adder using 3-to-8 line decoder and

- (a) two OR gates
- (b) two NOR gates

a)

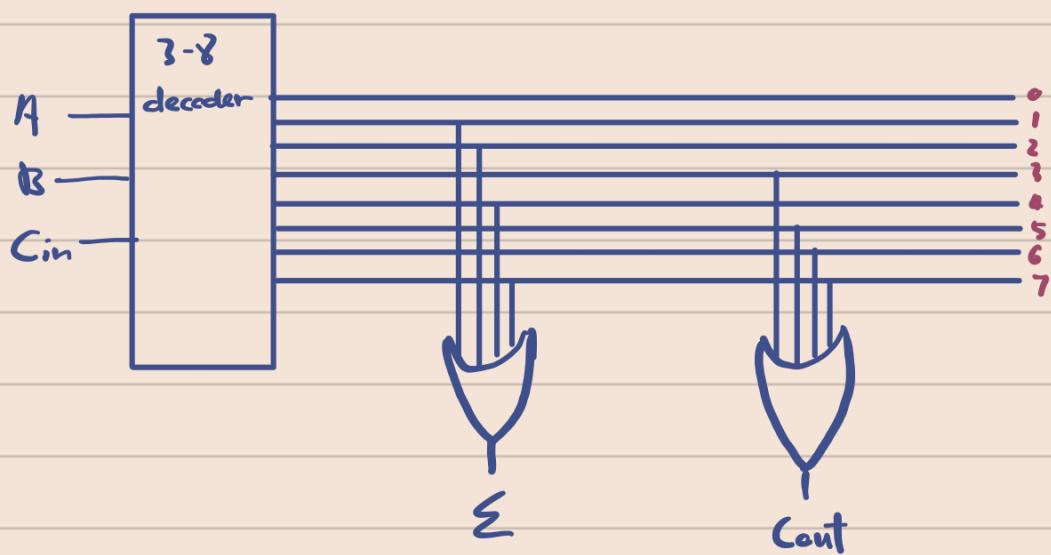

0	0	0	0	0	0	0	0
0	0	1	1	1	1	0	0
0	1	0	1	0	1	0	1
0	1	1	0	0	0	1	0
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	1
1	1	0	0	0	0	1	1
1	1	1	1	1	1	1	1

$\Sigma \quad C_{out}$

b)

